
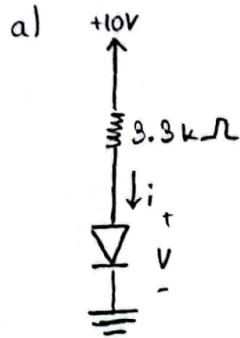



Q1)

Find the values of  $I$  and  $V$  for the circuits, assuming that the diodes are ideal.


Assume diode is off state;

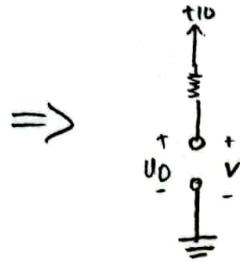

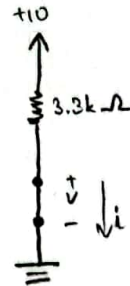
$i = 0$  } If diode is off,  $V_D$  must be negative.  
 $V_D = 10V$  } But, this condition is not satisfied.  
 So, diode is on state



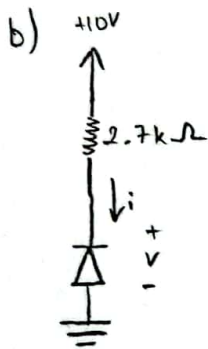Answer  
 $I = V/R \Rightarrow \frac{10}{3.3 \times 10^3} = 3.03 \text{ mA}$   
 Answer  
 $V = 10V$




Assume diode is off state;

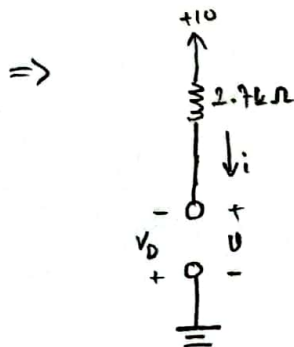


$i = 0$  } If diode is off,  $V_D < 0$ .  
 $V_D = -10V$  } Condition satisfied

Answer

$I = 0 \text{ A}$   
 $V = 10V$

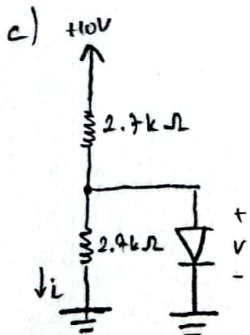


Assume diode is on state

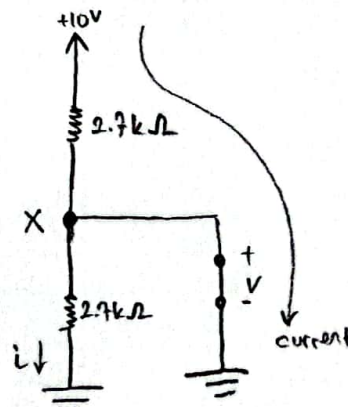 $V_x = 0$ , so  $I$  must be equal to 0 $V = 0$ 


Answer

$i = 0$   
 $V = 0$

d)

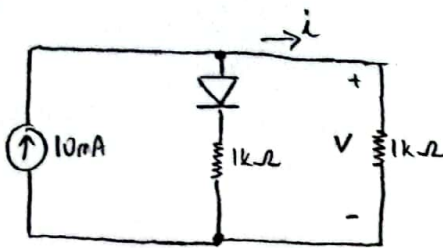

Assume diode is on

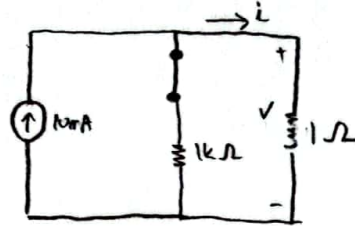

$V_D = 0$   $i > 0$ ; condition satisfied


$$R_{eq} \Rightarrow \frac{1}{\frac{1}{10^3} + 1} = 999 \text{ m}\Omega$$

$$V = 10 \times 10^{-3} \times 999 \times 10^{-3} = \boxed{9.99 \times 10^{-3} \text{ V}}$$


$$i = V/R \rightarrow \frac{9.99 \times 10^{-3}}{1} = \boxed{9.99 \text{ mA}}$$

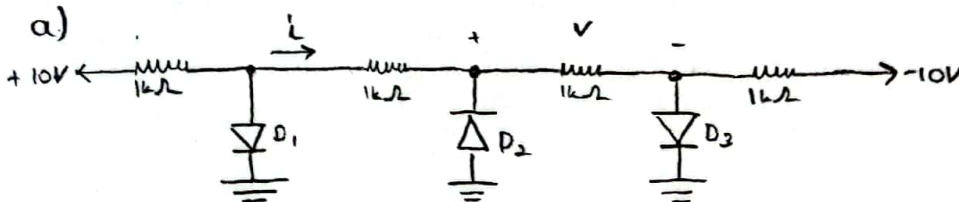Q2

Find the values of  $I$  and  $V$  for the circuits, assuming that diodes are ideal. For part (b), consider  $V_{in} = 0, 2, 6$  and  $10\text{V}$ . Also, plot  $V$  versus  $V_{in}$  for  $V_{in}$  ranging from  $-10\text{V}$  to  $10\text{V}$ .



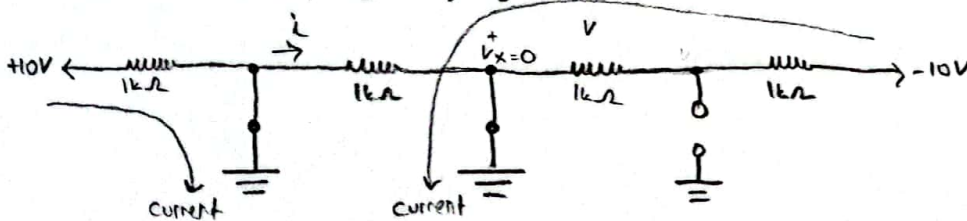Assume  $D_1$  on,  $D_2$  on,  $D_3$  off




$i$  must be equal to zero.

$$V = \frac{V_x - (-10\text{V})}{2\text{k}\Omega} \Rightarrow V = 5\text{V}$$


Answer

$$\left\{ \begin{array}{l} i = 0 \\ V = 5\text{V} \end{array} \right.$$


b)

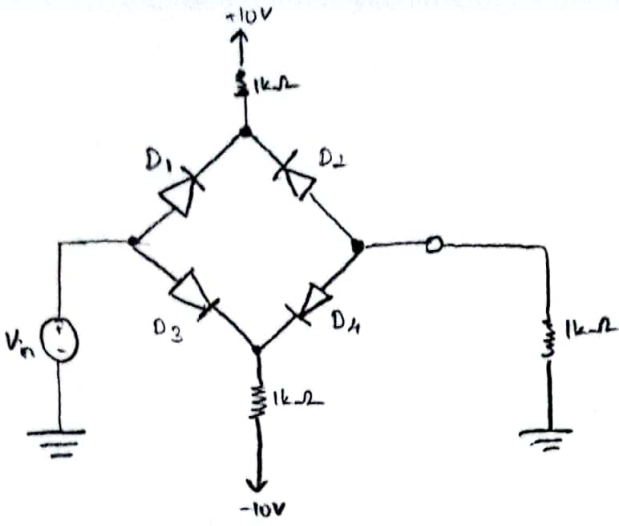

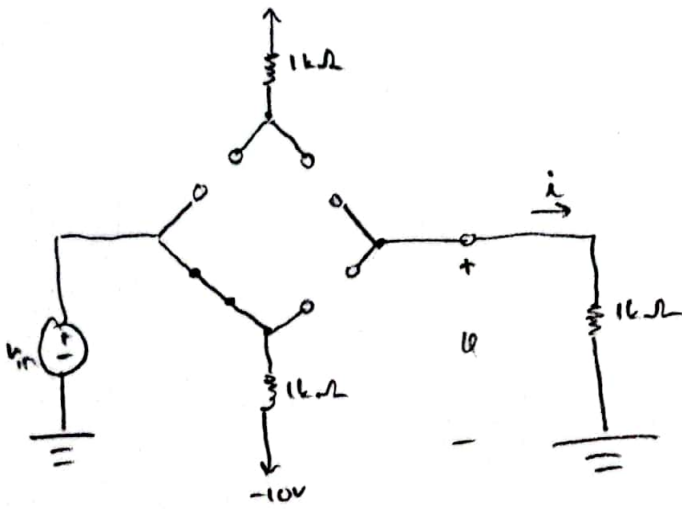$0 < V_{in} < 10$  iken, sadece  $D_3$  on durumunda olur.



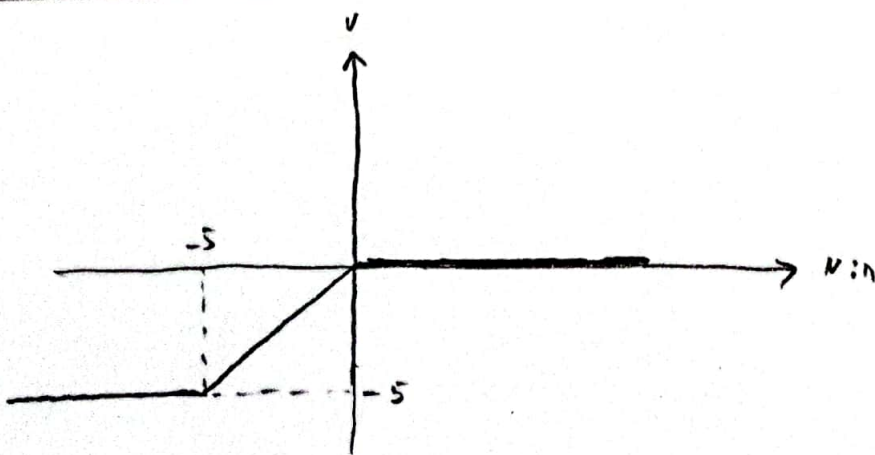Bu yüzden  $V_{in} = 0, 2, 4, 6, 8$  V değerleri için  $i = 0$   $V = 0$  olur




$V_{in} < 0$  iken  $D_3$  ve  $D_4$  on durumunda olur.

-5 değerinde iken  $D_3$  ve  $D_4$  tam iletkan hale gelir ve devredeki akım bu noktada sabitlenir




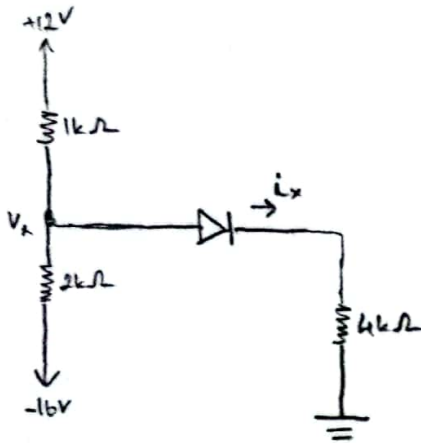Q3,

The diode is ideal. Determine the state of the diode and the values of  $V_x$  and  $i_x$ .



Assume diode on state;

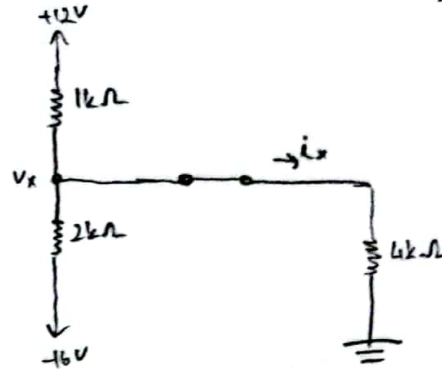

$$\frac{12 - V_x}{10^3} = \frac{V_x + 16}{2 \times 10^3} + \frac{V_x}{4 \times 10^3} \Rightarrow 48 - 4V_x = 2V_x + 32 + V_x$$

$$16 = 7V_x \Rightarrow V_x = 2.28V$$


$$i_x = \frac{V_x}{4 \times 10^3} \Rightarrow \frac{2.28}{4 \times 10^3} = 0.57mA$$

Answer

$$i_x > 0, \text{ so } \boxed{\text{diode is on, } V_x = 2.28V, i_x = 0.57mA}$$

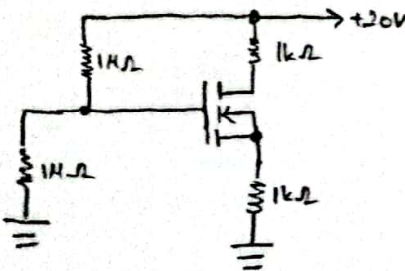Q4,

Find the values of  $I_{DQ}$  for the circuit. Assume that  $V_{to} = 4V$  and  $K = 1mA/V^2$ . Repeat for  $V_{to} = 2V$  and  $K = 2mA/V^2$ .



For  $V_{to} = 4V$  and  $K = 1 \times 10^{-3}A$ ,

$$V_G = 20 \times \frac{1k\Omega}{1k\Omega + 1k\Omega} \Rightarrow 10V$$

$$\text{At point Q} \Rightarrow V_G = V_{GSA} + I_{DQ} \cdot 10^3$$

$$\text{At saturation} \Rightarrow I_{DQ} = K(V_{GSA} - V_{to})^2$$

$$\Rightarrow 10 = V_{GSA} + 10^{-3} \cdot 10^3 (V_{GSA} - 4)^2 \Rightarrow y^2 + 16 - 8y + y = 10 \Rightarrow y^2 - 7y + 6 = 0$$

$$(y-1)(y-6) \Rightarrow y = 1/6$$

$$\boxed{V_{GSA} = 1 \text{ or } 6}$$

At saturation:  $V_{GSA} > V_{to}$

$$\text{So } V_{GSA} = 6$$

$$I_{DQ} = 10^{-3} (6 - 4)^2 \Rightarrow 4mA$$

Answer

b) for  $V_{to} = 2V$  and  $K = 2mA/V^2$ ,

$$V_{GS} = 10V$$

$$V_G = V_{GSQ} + I_{DQ} \cdot 10^3$$

$$I_{DQ} = K(V_{GSQ} - V_{to})^2$$

$$\left. \begin{array}{l} V_{GS} = 10V \\ V_G = V_{GSQ} + I_{DQ} \cdot 10^3 \\ I_{DQ} = K(V_{GSQ} - V_{to})^2 \end{array} \right\} \begin{array}{l} 10 = V_{GSQ} + 2(V_{GSQ} - 2)^2 \Rightarrow 10 = y + 2y^2 - 8y + 8 \\ \Rightarrow 2y^2 - 7y - 2 = 0 \quad \Delta = 49 - 4 \cdot 2 \cdot (-2) = 65 \end{array}$$

$$y_1 = \frac{7 + \sqrt{65}}{4} = 3.76$$

$$y_2 = \frac{7 - \sqrt{65}}{4} = -0.26$$


On saturation,

$$V_{GSQ} > V_{to}, \text{ so } V_{GSQ} = 3.76$$

$$I_{DQ} = 2 \times 10^{-3} (3.76 - 2)^2 = \boxed{6.19mA} \quad \text{Answer}$$

Q5.

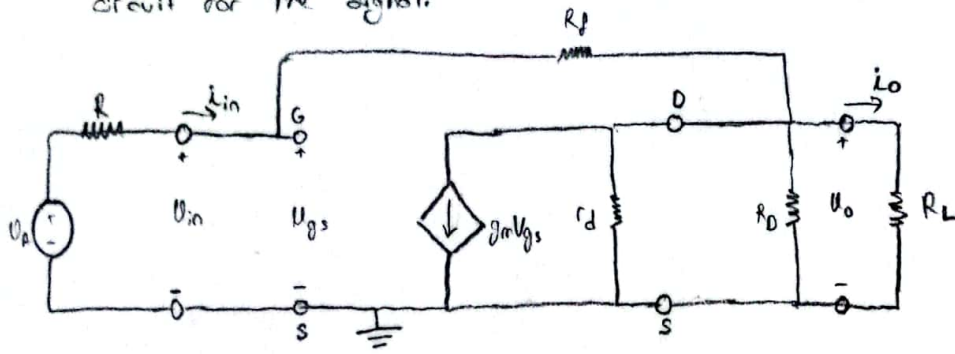a) Draw the small-signal equivalent circuit, assuming that the capacitors are short circuit for the signal.



b) Assume that  $r_d = \infty$ , and derive expressions for the voltage gain, input resistance, output resistance.

$$\frac{V_{in} - V_o}{R_g} = g_m \overbrace{V_{gs}}^{V_{in} = V_{gs}} + \frac{V_o}{R_L} \Rightarrow R_L' = \frac{1}{\cancel{\frac{1}{r_d}} + \frac{1}{R_D} + \frac{1}{R_L}} = \frac{1}{\frac{1}{R_D} + \frac{1}{R_L}}$$

$$V_{in} \left( \frac{1}{R_g} - g_m \right) = V_o \left( \frac{1}{R_g} + \frac{1}{R_D + R_L} \right)$$

$$A_v = \frac{V_o}{V_{in}} \Rightarrow \frac{\frac{1}{R_g} - g_m}{\frac{1}{R_g} + \frac{1}{R_D + R_L}}$$

Answer of voltage gain.

$$R_{in} = \frac{V_{in}}{i_{in}} \Rightarrow i_{in} = \frac{V_{in} - V_o}{R_g} \Rightarrow R_{in} = \frac{V_{in}}{\frac{V_{in} - V_o}{R_g}} \quad \text{Answer of input resistance}$$

$$R_o = \frac{R_D R_L (R_g + R)}{(R_g + R)(R_L + R_D) + (1 + g_m R)(R_D R_L)}$$

Answer



c) Find  $I_{DQ}$  if  $R = 100k\Omega$ ,  $R_g = 100k\Omega$ ,  $R_D = 3k\Omega$ ,  $R_L = 10k\Omega$ ,  $V_{DD} = 20V$ ,  $V_{t0} = 5V$ , and  $K = 1mA/V^2$ . Determine the value of  $g_m$  at the Q point.

$$V_{GS} = V_{DA}$$

$$\frac{20 - V_D}{R_D} = I_D$$

On saturation

$$I_D = \frac{K}{2} (V_{GS} - V_{t0})^2$$

$$\frac{20 - V_D}{3 \times 10^3} = \frac{10^{-3}}{2} (V_D - 5)^2$$

$$40 - 2V_D = 3V_D^2 + 75 - 30V_D$$

$$\Rightarrow 3V_D^2 - 28V_D + 35 = 0 \rightarrow V_D = 7.846$$

$$I_D = \frac{20 - 7.846}{3 \times 10^3} = 4.05 mA \quad \text{Answer}$$

$$g_m = \sqrt{2KI_D} = \sqrt{2 \times 10^{-3} \times 4.05 \times 10^{-3}} = 2.84 mA/V^2$$

d) Evaluate the exp. found in part (b) by using the values given part (c)

$$A_v = \frac{\frac{1}{R_g} - g_m}{\frac{1}{R_g} + \frac{1}{\frac{1}{R_D} + \frac{1}{R_L}}} \Rightarrow \frac{\frac{1}{100 \times 10^3} - 2.84 \times 10^{-3}}{\frac{1}{100 \times 10^3} + \frac{1}{\frac{1}{3 \times 10^3} + \frac{1}{10 \times 10^3}}} \Rightarrow \frac{-2.83 \times 10^{-3}}{4.33 \times 10^{-4}} = -6.53 \quad \text{Answer}$$

$$R_{in} \Rightarrow \frac{3 \times 10^3 \times 10 \times 10^3 + 100 \times 10^3 (3 \times 10^3 + 10 \times 10^3)}{(3 \times 10^3 \times 10 \times 10^3 \times 2.46 \times 10^{-3} + 3 \times 10^3 + 10 \times 10^3)} = 13.51 \times 10^3 \Omega \quad \text{Answer}$$

$$R_{out} \Rightarrow \frac{3 \times 10^3 \times 10 \times 10^3 (100 \times 10^3 + 100 \times 10^3)}{(100 \times 10^3 + 100 \times 10^3) (3 \times 10^3 + 10 \times 10^3) + (1 + 2.446 \times 100) 3 \times 10^3 \times 10 \times 10^3} = 537.2 \Omega \quad \text{Answer}$$

e) Find  $V_o(t)$  if  $V_i(t) = 0.2 \sin(200\pi t)$

$$\frac{V_o(t)}{V_i(t)} = -0.761$$

$$V_o(t) = -0.761 \times 0.2$$


$$V_o(t) = -0.152 \sin(200\pi t)$$

f) inverter. Çünkü output pozitiften  $\rightarrow$  negative dönüyor



Q6,

Find the currents and the region of operation for each of the enhancement transistors, for  $V_{in} = 0$  and  $V_{in} = 5V$ .  $|V_{th}| = 1V$  and  $K = 0.2mA/V^2$

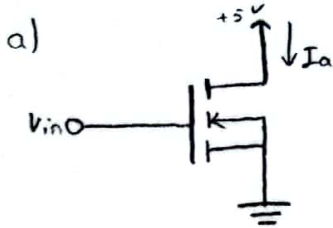

for  $V_{in} = 0V$ ,  $V_{th} = 1$

$$V_{GS} = 0V; V_{GS} < V_{th} \Rightarrow \boxed{\text{Cutoff region } I_a = 0}$$

Answer

for  $V_{in} = 5V$ ,  $V_{th} = 1$ ,  $V_{DS} = 5V$


$$V_{GS} = 5V; V_{GS} > V_{th} \text{ and } V_{DS} > V_{GS} - V_{th}$$

$$5 > 4 \Rightarrow \boxed{\text{Saturation region}}$$

$$I_a = K(V_{GS} - V_{th})^2 = 0.2 \times 10^{-3} (4)^2 = \boxed{3.2mA}$$

$$\boxed{\text{Saturation region, } I_a = 3.2mA}$$

Answer

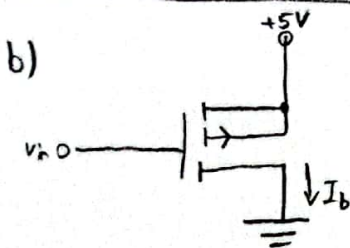

for  $V_{in} = 0V$ ,  $V_{th} = -1$

$$V_{GS} = -5V; V_{GS} \leq V_{th} \quad V_{DS} = -5V \text{ and } V_{DS} \leq V_{GS} - V_{th}$$

$$-5 \leq -4 \Rightarrow \boxed{\text{Saturation region}}$$

Answer

$$I_b = K(V_{GS} - V_{th})^2 \Rightarrow 0.2 \times 10^{-3} (-4)^2 = \boxed{3.2mA}$$

Answer

for  $V_{in} = 5V$ ,  $V_{th} = -1$

$$V_{GS} = 0V; V_{DS} = -5V \quad V_{GS} > V_{th} \Rightarrow \boxed{\text{Cutoff region}} \text{ and } \boxed{I_b = 0}$$

Answer      Answer